

CSC258 PRELAB 7

Tingfeng Xia


November 7, 2019

PART I

(9) I should first present my test cases, below is the writing that we will do. We will read from positions 00000, 01000, 10000, and 11100. The first three are the three boxes to the top left of the memory block above, while the last one 11100 is 28 in binary, corresponding to the bottom right box.

0	0	0	1	0	0	0	0
0	0	1	0	0	0	0	0
0	0	1	1	0	0	0	0
0	1	0	0	0	0	0	0

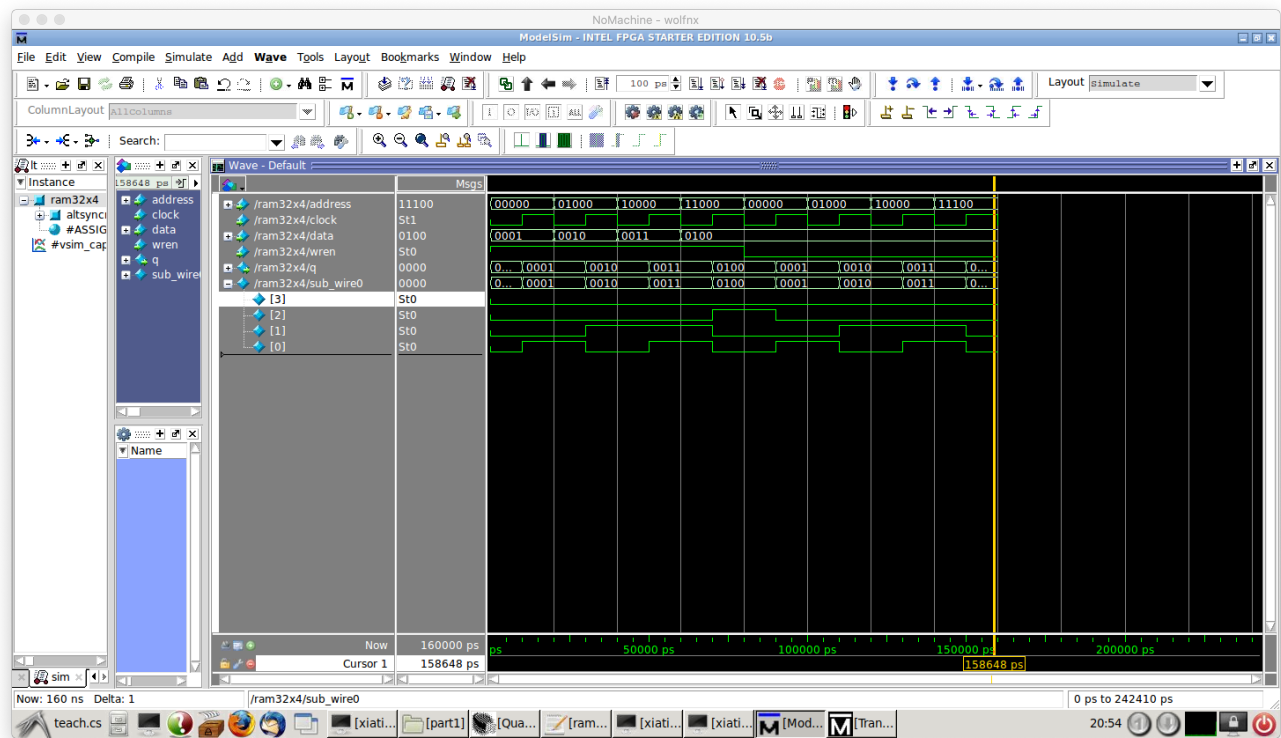Indeed, we have the following in the ModelSim results for the `ram32x4.v` module that we just created.



(10) Here is my code that instantiates the `ram32x4.v` module from top level. Notice that this will only work if the `ram32x4.v` was included as part of the project. Here is my code

```
// SW[3:0] for data inputs
// SW[8:4] for address inputs
// SW[9] is write enable
// KEY[0] clock
```

```

// show address on HEX5 and HEX4
// input data on HEX2
// output data on HEX0 (output of memory)

module ram_toplv(
    input [9:0] SW,
    input [0:0] KEY,
    output [6:0] HEX5,
    output [6:0] HEX4,
    output [6:0] HEX2,
    output [6:0] HEX0
);
    wire [3:0] ramout;

    ram32x4 ram_block(
        .address(SW[8:4]),
        .clock(KEY[0]),
        .data(SW[3:0]),
        .wren(SW[9]),
        .q(ramout[3:0])
    );

    // The last bit, for hex5
    hex_decoder hex5({3'b000, SW[8]}, HEX5[6:0]);
    hex_decoder hex4(SW[7:4], HEX4[6:0]);
    hex_decoder hex2(SW[3:0], HEX2[6:0]);
    hex_decoder hex0(ramout[3:0], HEX0[6:0]);

endmodule



// borrowed from lab6 starter code
module hex_decoder(hex_digit, segments);
    input [3:0] hex_digit;
    output reg [6:0] segments;

    always @(*)
        case (hex_digit)
            4'h0: segments = 7'b100_0000;
            4'h1: segments = 7'b111_1001;
            4'h2: segments = 7'b010_0100;
            4'h3: segments = 7'b011_0000;
            4'h4: segments = 7'b001_1001;
            4'h5: segments = 7'b001_0010;
            4'h6: segments = 7'b000_0010;
            4'h7: segments = 7'b111_1000;
            4'h8: segments = 7'b000_0000;
            4'h9: segments = 7'b001_1000;
            4'hA: segments = 7'b000_1000;
            4'hB: segments = 7'b000_0011;
            4'hC: segments = 7'b100_0110;
            4'hD: segments = 7'b010_0001;
            4'hE: segments = 7'b000_0110;
            4'hF: segments = 7'b000_1110;
            default: segments = 7'h7f;
        endcase
endmodule

```

endmodule

(11) Here is the schematic for the design

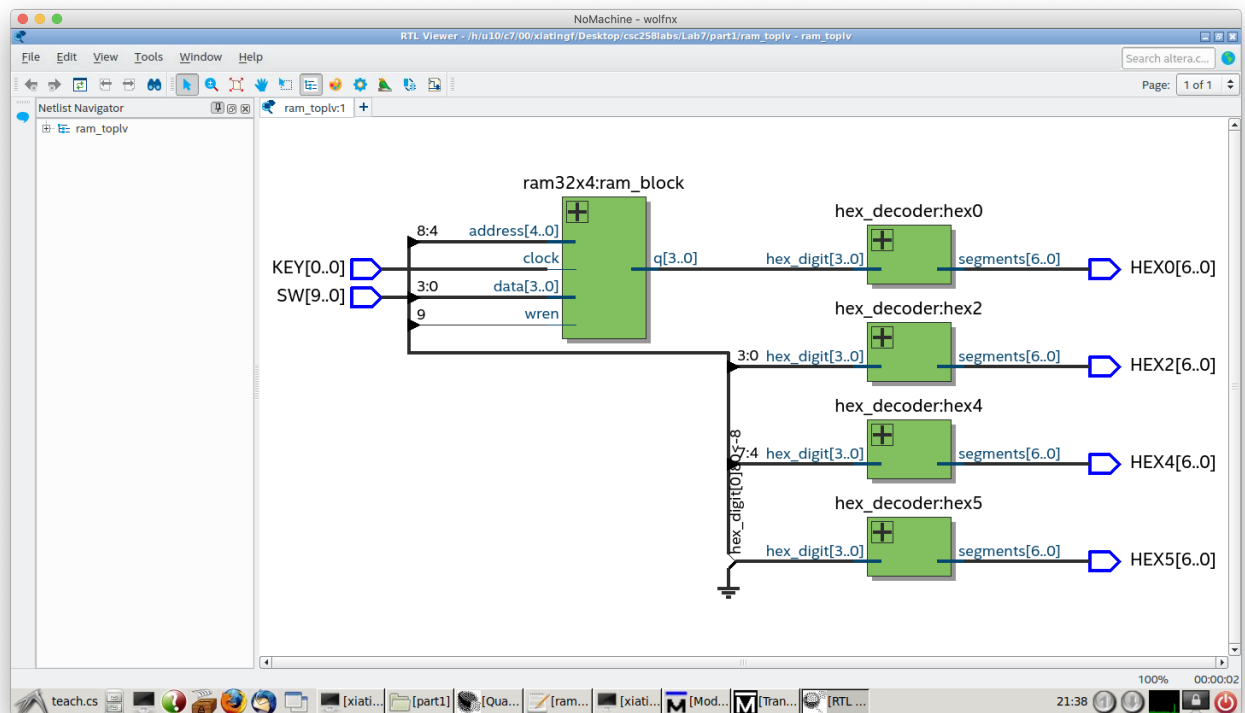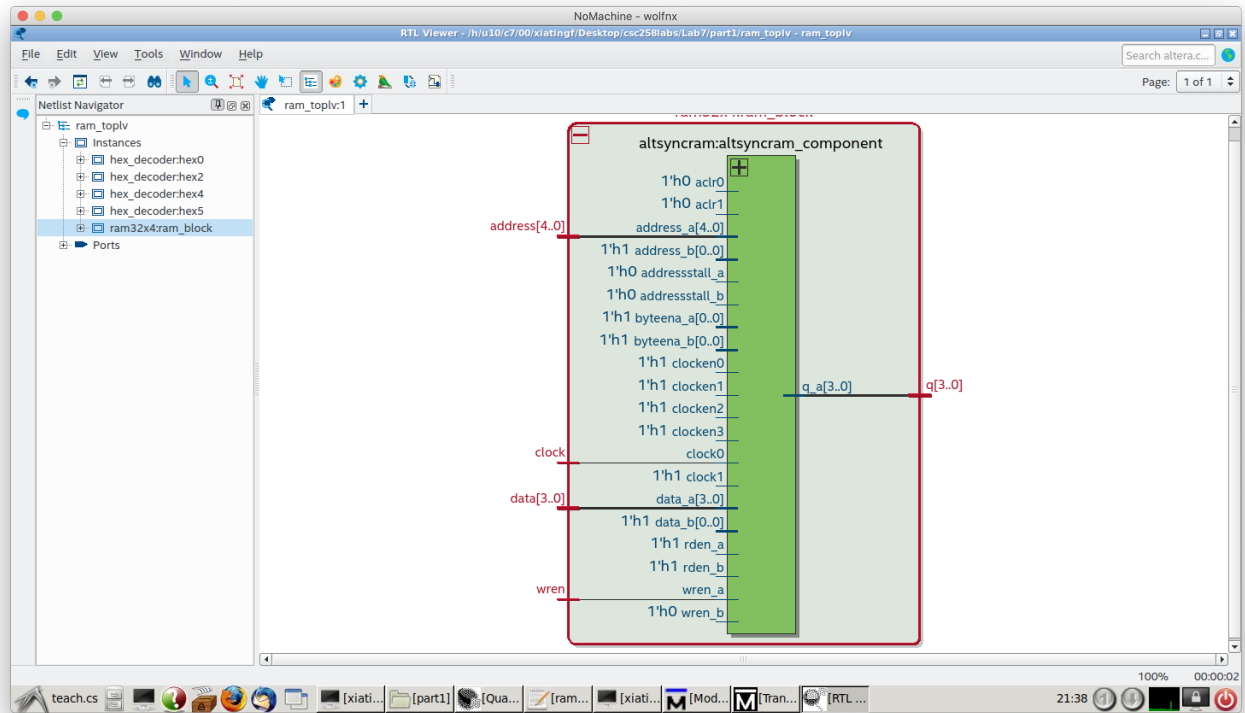

PART II

(1) Here is my implementation of the datapath module

```
module datapath(  
    input clk, resetn, ld_x, ld_y, ld_color,  
    input [2:0] color_in,  
    input [6:0] coordinate,  
    output [7:0] x_out,  
    output [6:0] y_out,  
    output [2:0] color_out  
);  
  
    reg [7:0] x;  
    reg [6:0] y;  
    reg [2:0] color;  
    reg [2:0] x_pos;  
    reg [2:0] y_pos;  
  
    //reset or load  
    always @(posedge clk) begin  
        if (!resetn) begin  
            x <= 8'b0;  
            y <= 7'b0;  
            color <= 3'b0;  
        end  
        // the load signals tells if we are loading  
        // or we are just printing the square  
        else begin  
            if (ld_x)  
                x <= {1'b0, coordinate};  
            if (ld_y)  
                y <= coordinate;  
            if (ld_color)  
                color <= color_in;  
        end  
    end  
    //logic for drawing the square  
    always @(posedge clk) begin  
        if (~resetn) begin  
            x_pos <= 2'b00;  
            y_pos <= 2'b00;  
        end  
        else  
            if (x_pos == 2'b11 && y_pos == 2'b11) begin  
                x_pos <= 2'b00;  
                y_pos <= 2'b00;  
            end  
            else begin  
                if (x_pos == 2'b11) begin  
                    x_pos <= 2'b00;  
                    y_pos <= y_pos + 1'b1;  
                end  
                else begin  
                    x_pos <= x_pos + 1'b1;  
                end  
            end  
        end  
    end
```


```

end

assign x_out = x + x_pos[1:0];
assign y_out = y + y_pos[1:0];
assign color_out = color;
endmodule

```

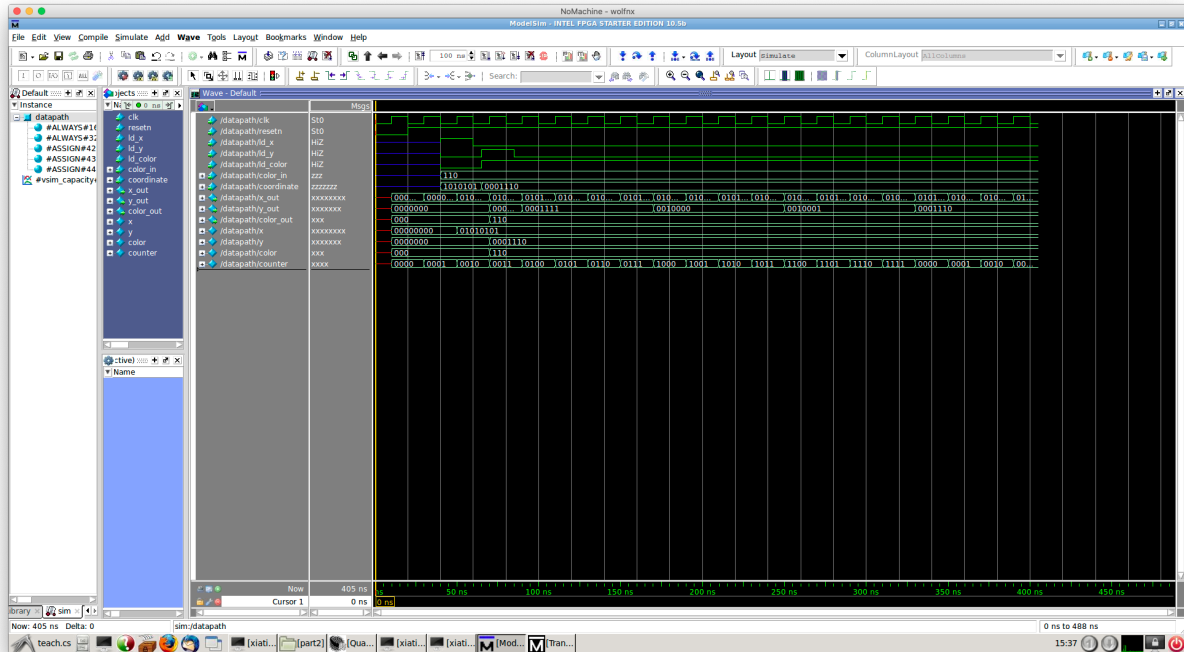Here is the ModelSim result for the datapath module, notice the box of size 4 by 4 is looped over in the x_out and y_out simulated.



(2) Here is my verilog module control, the FSM in the circuit

```

/// FSM module control, instantiation is c0
module control(
    input clk,
    input resetn,
    input load,
    input go,
    output reg ld_x,
    output reg ld_y,
    output reg ld_color,
    output reg writeEn);

    reg [2:0] current_state, next_state;

    localparam LOAD_X = 3'b000,
               LOAD_X_WAIT = 3'b001,
               LOAD_Y_C = 3'b010,
               LOAD_Y_C_WAIT = 3'b011,
               DO_PLOT = 3'b100;

    //reset
    always @(posedge clk) begin
        if (~resetn)
            current_state <= LOAD_X;
    end

```


```

        else
            current_state <= next_state;
        end
    //state table
    always @(*)
    begin: state_table
        case (current_state)
            LOAD_X: next_state = load ? LOAD_X_WAIT : LOAD_X;
            LOAD_X_WAIT: next_state = load ? LOAD_X_WAIT : LOAD_Y_C;
            LOAD_Y_C: next_state = go ? LOAD_Y_C_WAIT : LOAD_Y_C;
            LOAD_Y_C_WAIT: next_state = go ? LOAD_Y_C_WAIT : DO_PLOT;
            DO_PLOT: next_state = load ? LOAD_X : DO_PLOT;
            default: next_state = LOAD_X;
        endcase
    end

    always @(*)
    begin
        ld_x = 1'b0;
        ld_y = 1'b0;
        ld_color = 1'b0;
        writeEn = 0;
        case (current_state)
            LOAD_X: ld_x = 1;
            LOAD_X_WAIT: ld_x = 1;
            LOAD_Y_C: begin
                ld_x = 0;
                ld_y = 1;
                ld_color = 1;
            end
            LOAD_Y_C_WAIT: begin
                ld_x = 0;
                ld_y = 1;
                ld_color = 1;
            end
            DO_PLOT: writeEn = 1;
        endcase
    end
endmodule

```

 Here is the screenshot for the ModelSim results for the FSM, notice the states incrementing and the `next_state` is set as appropriate.



(c) In the below code, I instantiated the `control` module and the `datapath` as appropriate.

```
// Part 2 skeleton
module part2
(
    CLOCK_50, // On Board 50 MHz
    // Your inputs and outputs here
    KEY,
    SW,
    // The ports below are for the VGA output. Do not change.
    VGA_CLK, // VGA Clock
    VGA_HS, // VGA H_SYNC
    VGA_VS, // VGA V_SYNC
    VGA_BLANK_N, // VGA BLANK
    VGA_SYNC_N, // VGA SYNC
    VGA_R, // VGA Red[9:0]
    VGA_G, // VGA Green[9:0]
    VGA_B, // VGA Blue[9:0]
);

input          CLOCK_50; // 50 MHz
input [9:0]    SW;
input [3:0]    KEY;

// Declare your inputs and outputs here
// Do not change the following outputs
output          VGA_CLK; // VGA Clock
output          VGA_HS; // VGA H_SYNC
output          VGA_VS; // VGA V_SYNC
output          VGA_BLANK_N; // VGA BLANK
output          VGA_SYNC_N; // VGA SYNC
output [9:0]    VGA_R; // VGA Red[9:0]
output [9:0]    VGA_G; // VGA Green[9:0]
output [9:0]    VGA_B; // VGA Blue[9:0]
```

```

wire resetn;
assign resetn = KEY[0];

// Create the colour, x, y and writeEn wires that are inputs to the controller.
wire [2:0] colour;
wire [7:0] x;
wire [6:0] y;
wire writeEn;

// Create an Instance of a VGA controller - there can be only one!
// Define the number of colours as well as the initial background
// image file (.MIF) for the controller.
vga_adapter VGA(
    .resetn(resetn),
    .clock(CLOCK_50),
    .colour(colour),
    .x(x),
    .y(y),
    .plot(writeEn),
    /* Signals for the DAC to drive the monitor. */
    .VGA_R(VGA_R),
    .VGA_G(VGA_G),
    .VGA_B(VGA_B),
    .VGA_HS(VGA_HS),
    .VGA_VS(VGA_VS),
    .VGA_BLANK(VGA_BLANK_N),
    .VGA_SYNC(VGA_SYNC_N),
    .VGA_CLK(VGA_CLK));
defparam VGA.RESOLUTION = "160x120";
defparam VGA.MONOCHROME = "FALSE";
defparam VGA.BITS_PER_COLOUR_CHANNEL = 1;
defparam VGA.BACKGROUND_IMAGE = "black.mif";

// Put your code here. Your code should produce signals x,y,colour and writeEn/plot
// for the VGA controller, in addition to any other functionality your design may require.

// Instansiate datapath
datapath d0(
    .clk(CLOCK_50),
    .color_in(SW[9:7]),
    .resetn(resetn),
    .ld_x(ld_x),
    .ld_y(ld_y),
    .ld_color(ld_color),
    .coordinate(SW[6:0]),
    .x_out(x),
    .y_out(y),
    .color_out(colour)
);

// Instansiate FSM control
control c0(
    .clk(CLOCK_50),
    .resetn(resetn),
    .load(! (KEY[3])),

```




```

        .go(! (KEY[1])),
        .ld_x(ld_x),
        .ld_y(ld_y),
        .ld_color(ld_color),
        .writeEn(writeEn)
    );

```

```
endmodule
```

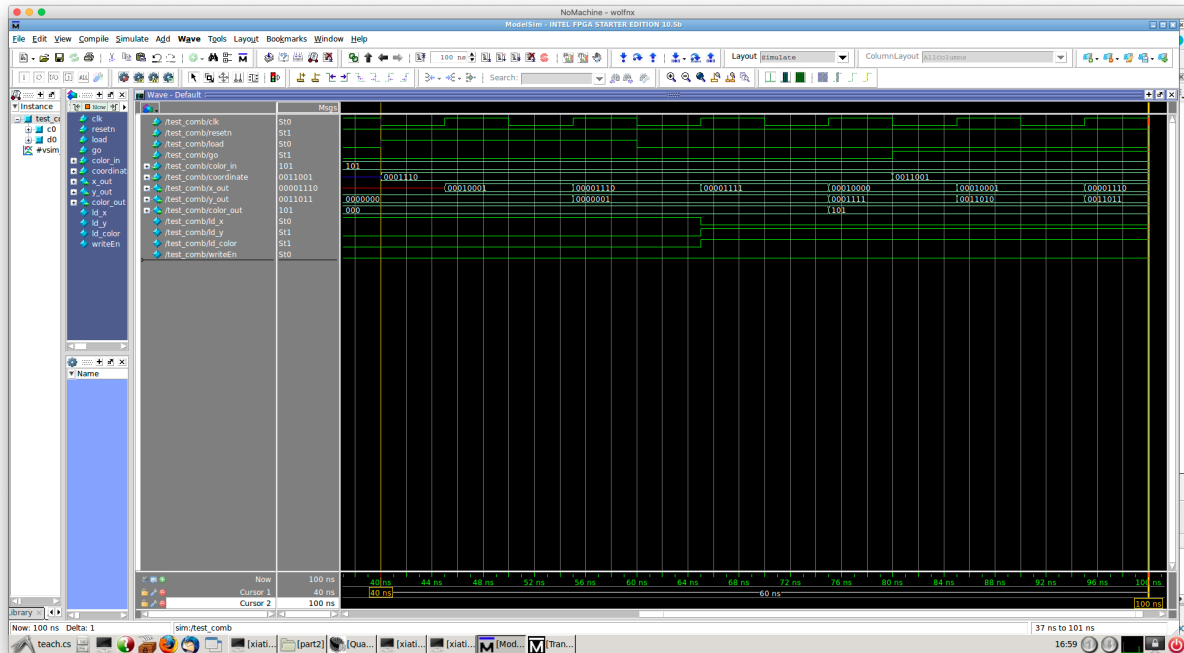But somehow model sim is complaining about missing modules when I try to simulate the above code, so I instantiated another module for the sake of testing the combination of FSM and datapath. Here is the result of the simulation.



Here is my code for this testing module

```

module test_comb(
    input clk, resetn, load, go,
    input [2:0] color_in,
    input [6:0] coordinate,
    output [7:0] x_out,
    output [6:0] y_out,
    output [2:0] color_out
);

    wire ld_x, ld_y, ld_color, writeEn;

    control c0(
        .clk(clk),
        .resetn(resetn),
        .load(load),
        .go(go),
        .ld_x(ld_x),
        .ld_y(ld_y),
        .ld_color(ld_color),

```

```
        .writeEn(writeEn)
    );

    datapath d0(
        .clk(clk),
        .color_in(color_in[2:0]),
        .resetn(resetn),
        .ld_x(ld_x),
        .ld_y(ld_y),
        .ld_color(ld_color),
        .coordinate(coordinate[6:0]),
        .x_out(x_out),
        .y_out(y_out),
        .color_out(color_out)
    );

endmodule
```

PART III