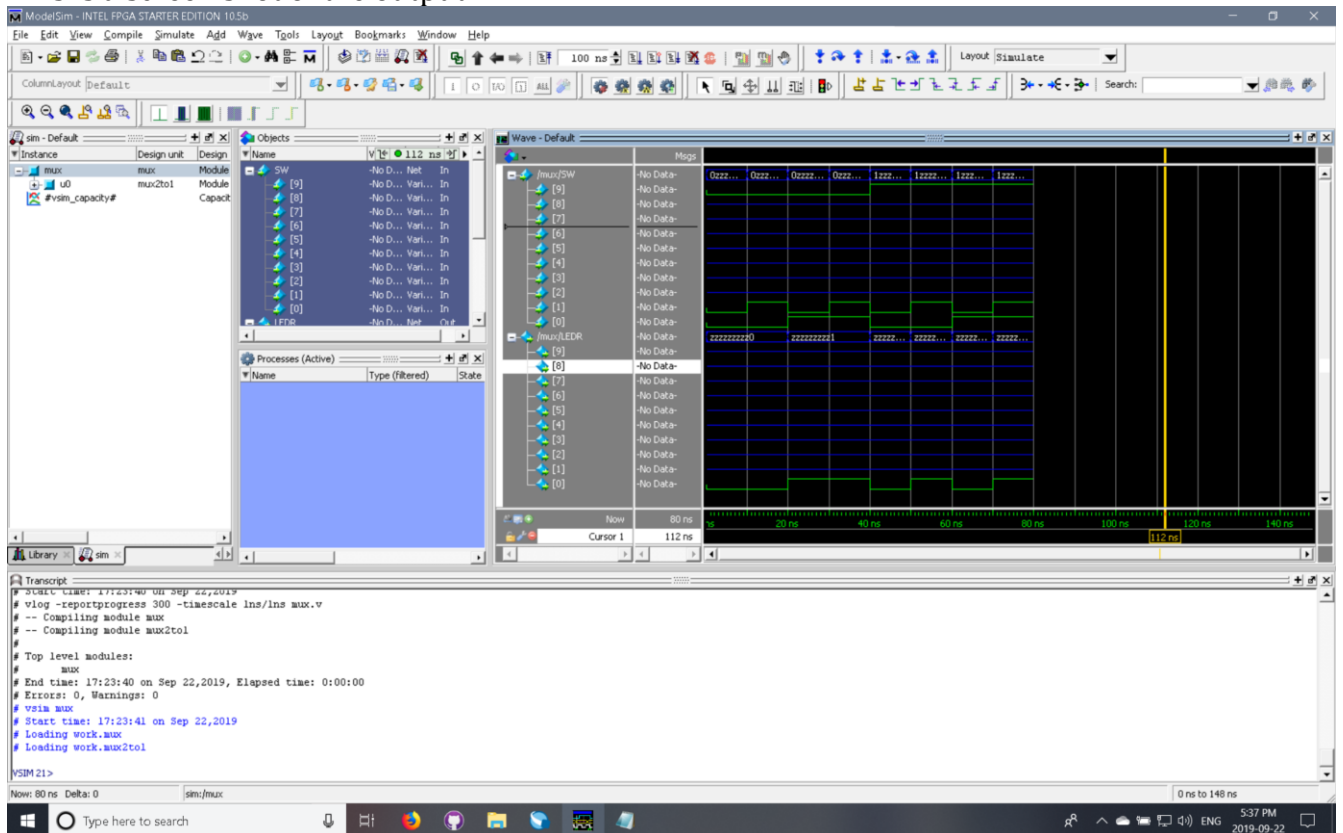


# CSC258 LAB2 PRELAB

TINGFENG XIA, 1003780884, xiatingf

## 5 PART I

1. This is a screen shot of the output.




SW[0] (x)	SW[1] (y)	SW[9] (s)	LEDR[0] (m)
0	0	0	0
0	1	0	0
1	0	0	1
1	1	0	1
0	0	1	0
0	1	1	1
1	0	1	0
1	1	1	1

According to the results above, we can confirm that the design is working properly since when SW[9], i.e. input s, is zero, the output m is equal to SW[0] which is our x input and when SW[9] is 1, the output m is equal to the y input(SE[1]). So the multiplexer is correct.

## 6 PART II

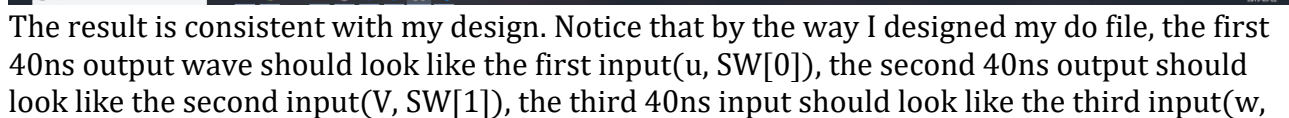1. Here we have 6 inputs in total to consider, so there would be  $2^6 = 64$  rows in a full truth table.
2. Here is my design (Notice that I assumed the mux2to1 multiplexer to have the same input/output layout as specified in the handout.)



SW[2]) and the last 40ns input should look like the fourth input(x, SW[3]). The output that I got from LEDR[0] is exactly what I expected so I am confident that my circuit is working correctly.

## 7 PART III

1. First, let's write down the full truth table (Notice that here 0 marks emitting light)

hex.	C <sub>3</sub>	C <sub>2</sub>	C <sub>1</sub>	C <sub>0</sub>	HEX[0]	HEX[1]	HEX[2]	HEX[3]	HEX[4]	HEX[5]	HEX[6]
0	0	0	0	0	0	0	0	0	0	0	1
1	0	0	0	1	1	0	0	1	1	1	1
2	0	0	1	0	0	0	1	0	0	1	0
3	0	0	1	1	0	0	0	0	1	1	0
4	0	1	0	0	1	0	0	1	1	0	0
5	0	1	0	1	0	1	0	0	1	0	0
6	0	1	1	0	0	1	0	0	0	0	0
7	0	1	1	1	0	0	0	1	1	1	1
8	1	0	0	0	0	0	0	0	0	0	0
9	1	0	0	1	0	0	0	0	1	0	0
A	1	0	1	0	0	0	0	1	0	0	0
B	1	0	1	1	1	1	0	0	0	0	0
C	1	1	0	0	0	1	1	0	0	0	1
D	1	1	0	1	1	0	0	0	0	1	0
E	1	1	1	0	0	1	1	0	0	0	0
F	1	1	1	1	0	1	1	1	0	0	0

#NOTATION: For the following 7 tables and expressions, by  $\overline{AB}$  I mean  $\overline{A}\overline{B}$ , this was to simplify the typesetting.

- a. For HEX[0], we have the Karnaugh map

	$\overline{c_1}\overline{c_0}$	$\overline{c_1}c_0$	$c_1c_0$	$c_1\overline{c_0}$
$\overline{c_3}\overline{c_2}$	0	1	0	0
$\overline{c_3}c_2$	1	0	0	0
$c_3\overline{c_2}$	0	1	0	0
$c_3c_2$	0	0	1	0

Thus,  $HEX[0] = \overline{c_3}c_2\overline{c_1}c_0 + \overline{c_3}c_2\overline{c_1}\overline{c_0} + c_3c_2\overline{c_1}c_0 + c_3\overline{c_2}c_1c_0$

- b. For HEX[1], we have the Karnaugh map

	$\overline{c_1}\overline{c_0}$	$\overline{c_1}c_0$	$c_1c_0$	$c_1\overline{c_0}$
$\overline{c_3}\overline{c_2}$	0	0	0	0
$\overline{c_3}c_2$	0	1	0	1
$c_3\overline{c_2}$	1	0	1	1
$c_3c_2$	0	0	1	0

Thus,  $HEX[1] = \overline{c_3}c_2\overline{c_1}c_0 + c_3c_1c_0 + c_2c_1\overline{c_0} + c_3c_2\overline{c_0}$

- c. For HEX[2], we have the Karnaugh map

	$\overline{c_1}\overline{c_0}$	$\overline{c_1}c_0$	$c_1c_0$	$c_1\overline{c_0}$
$\overline{c_3}\overline{c_2}$	0	0	0	1
$\overline{c_3}c_2$	0	0	0	0

$c_3c_2$	1	0	1	1
$c_3\bar{c}_2$	0	0	0	0

Thus,  $HEX[2] = c_3c_2\bar{c}_0 + c_3c_2c_1 + \bar{c}_3\bar{c}_2c_1\bar{c}_0$

- d. For  $HEX[3]$ , we have the Karnaugh map

	$\bar{c}_1\bar{c}_0$	$\bar{c}_1c_0$	$c_1c_0$	$c_1\bar{c}_0$
$\bar{c}_3\bar{c}_2$	0	1	0	0
$\bar{c}_3c_2$	1	0	1	0
$c_3c_2$	0	0	1	0
$c_3\bar{c}_2$	0	0	0	1

Thus,  $HEX[3] = \bar{c}_3c_2\bar{c}_1\bar{c}_0 + \bar{c}_3\bar{c}_2\bar{c}_1c_0 + c_2c_1c_0 + c_3\bar{c}_2c_1\bar{c}_0$

- e. For  $HEX[4]$ , we have the Karnaugh map

	$\bar{c}_1\bar{c}_0$	$\bar{c}_1c_0$	$c_1c_0$	$c_1\bar{c}_0$
$\bar{c}_3\bar{c}_2$	0	1	1	0
$\bar{c}_3c_2$	1	1	1	0
$c_3c_2$	0	0	0	0
$c_3\bar{c}_2$	0	1	0	0

Thus,  $HEX[4] = \bar{c}_3c_0 + \bar{c}_2\bar{c}_1c_0 + \bar{c}_3c_2\bar{c}_1$

- f. For  $HEX[5]$ , we have the Karnaugh map

	$\bar{c}_1\bar{c}_0$	$\bar{c}_1c_0$	$c_1c_0$	$c_1\bar{c}_0$
$\bar{c}_3\bar{c}_2$	0	1	1	1
$\bar{c}_3c_2$	0	0	1	0
$c_3c_2$	0	1	0	0
$c_3\bar{c}_2$	0	0	0	0

Thus,  $HEX[5] = \bar{c}_3\bar{c}_2c_0 + \bar{c}_3\bar{c}_2c_1 + \bar{c}_3c_1c_0 + c_3c_2\bar{c}_1c_0$

- g. For  $HEX[6]$ , we have the Karnaugh map

	$\bar{c}_1\bar{c}_0$	$\bar{c}_1c_0$	$c_1c_0$	$c_1\bar{c}_0$
$\bar{c}_3\bar{c}_2$	1	1	0	0
$\bar{c}_3c_2$	0	0	1	0
$c_3c_2$	1	0	0	0
$c_3\bar{c}_2$	0	0	0	0

Thus,  $HEX[6] = \bar{c}_3\bar{c}_2\bar{c}_1 + \bar{c}_3c_2c_1c_0 + c_3c_2\bar{c}_1\bar{c}_0$

- Please see the hexdecoder.v file
- Here is a screenshot of the output, please see the hexdecoder.do file for the test code, notice that here we are using BA3165 which is the lab name for the test.

